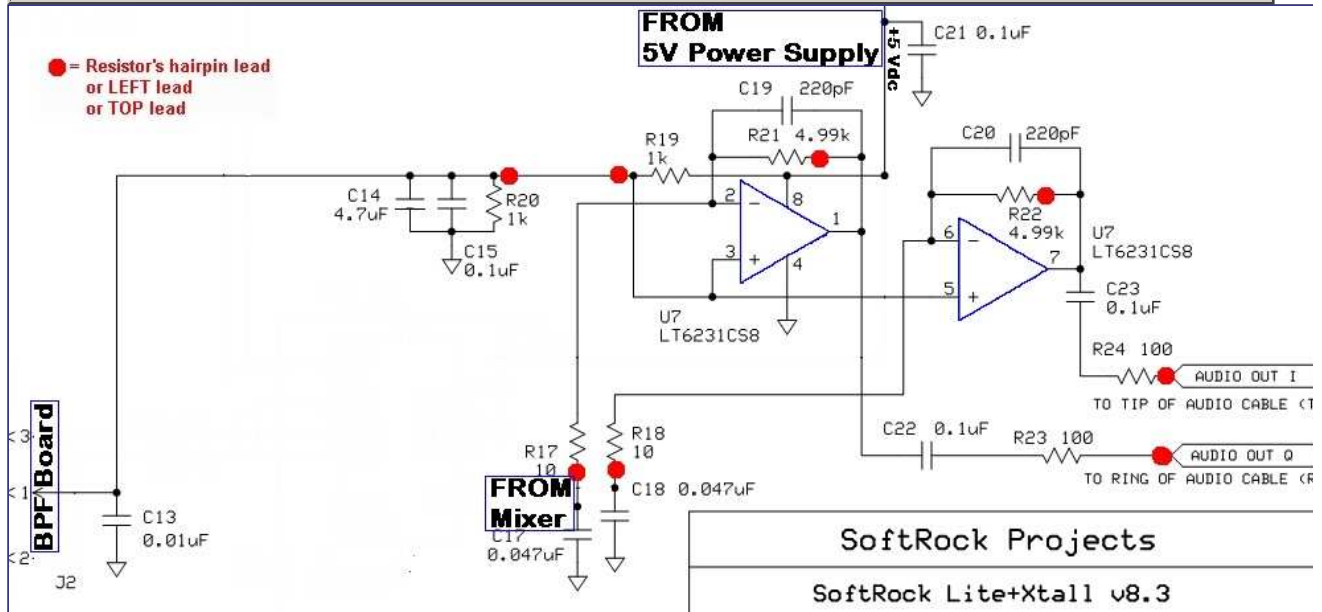


IV - Op Amps Stage

Home Page Power Supply Local Oscillator Dividers Op Amps BPF(s) Mixer Comments

Schematic



Theory of Operation

This stage amplifies the quadrature audio frequency difference products from the Mixer stage via R17 and R18.

R19 and R20 make up a voltage divider that provides the 2.5 Vdc bias to the Op-Amps, configured as an inverting amplifier. The ratios of R21/R17 and R22/R18, respectively, determine the voltage gain of the output over the input for each Op-Amp. That voltage gain is theoretically 499:1, or about 54 dB. Each Op-Amp's output is capacitively coupled through a 100 ohm resistor to the "Ring" (Q) and "Tip" (I) Audio Out terminals for input to the PC's sound card.

Summary Build Steps

- Install SMT Capacitors (5)
- Install U7
- Install resistors (8)
- Install ceramic caps (5)
- [Testing](#)

Bill of Materials

Designation	Component	Type	Qty	Notes
C13	0.01 µF	SMT 1206	1	
C14	4.7 µF	ceramic	1	code 475
C15	0.1 µF	SMT 1206	1	
C17	0.047 µF	ceramic	1	code 473
C18	0.047 µF	ceramic	1	code 473
C19	220 pF	ceramic	1	code 221
C20	220 pF	ceramic	1	code 221
C21	0.1 µF	SMT 1206	1	
C22	0.1 µF	SMT 1206	1	
C23	0.1 µF	SMT 1206	1	
R17	10 Ohm	Resistor 1%	1	hairpin (west-east)
R18	10 Ohm	Resistor 1%	1	hairpin (west-east)
R19	1k Ohm	Resistor 1%	1	Hairpin (south - North)
R20	1k Ohm	Resistor 1%	1	hairpin (east- west)
R21	4.99k Ohm	Resistor 1%	1	hairpin (east- west)
R22	4.99k Ohm	Resistor 1%	1	hairpin (east- west)
R23	100 Ohm	Resistor 1%	1	hairpin (north-south)
R24	100 Ohm	Resistor 1%	1	Hairpin (south - North)


U7	LT6231	SOIC-8 OpAmp	1	(bottom)
n/a	5 μ F	ceramic	1	blocking capacitor for audio test (not furnished with kit)

Installation Notes

This stage mainly adds the amplification capabilities via the dual LT6231 Operational Amplifier, U7. The builder must take necessary [ESD precautions](#). See the [guidelines on installing SMT ICs](#).

Bottomside Components

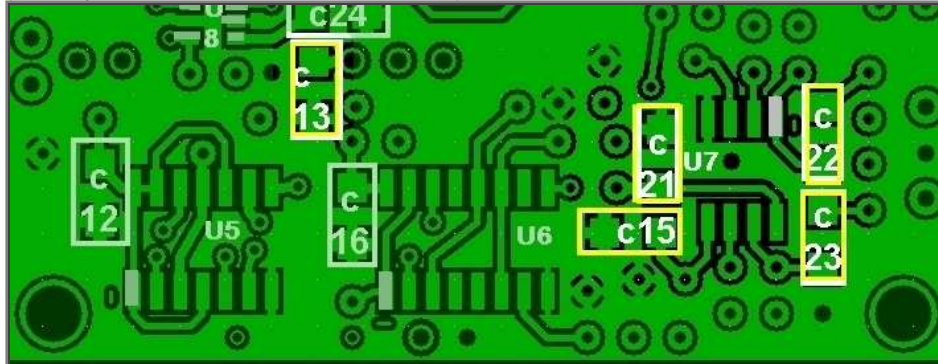(You may want to refer to the [board bottom view](#))



Install the SMT capacitors

- Install the 0.01 μ F SMT cap, C13 (from the unmarked strip)
- Install the four 0.1 μ F SMT caps: C15, C21-23 C (from the strip with the black marking).

Check	Designation	Component	Type
	C13	0.01 μ F	SMT 1206
	C15	0.1 μ F	SMT 1206 (black-marked strip)
	C21	0.1 μ F	SMT 1206 (black-marked strip)
	C22	0.1 μ F	SMT 1206 (black-marked strip)
	C23	0.1 μ F	SMT 1206 (black-marked strip)

Install U7

(see notes on [ESD precautions](#) and [SMT IC Installation](#))


- Install U7, the LT6231 Operational Amplifier, on the bottom of the board

Check	Designation	Component	Orientation
	U7	LT6231	
			SOIC-8 OpAmp

Topside Components

Install Resistors

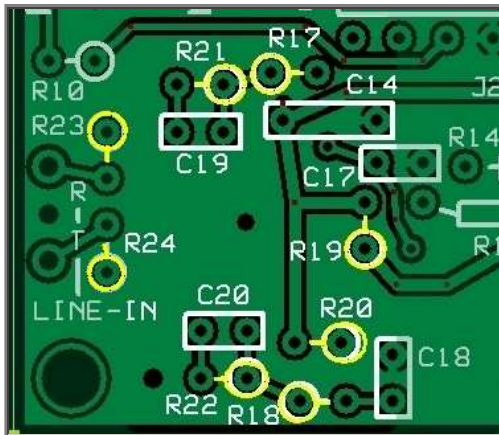
- Install resistors R17-R24 (observe the correct "hairpin" orientation - see table below).



Check	Designation	Component	Type	Component Orientation
	R17	10 Ohm	Resistor 1%	hairpin (west-east)
	R18	10 Ohm	Resistor 1%	hairpin (west-east)
	R19	1k Ohm	Resistor 1%	Hairpin (south - North)
	R20	1k Ohm	Resistor 1%	hairpin (east- west)
	R21	4.99k Ohm	Resistor 1%	hairpin (east- west)
	R22	4.99k Ohm	Resistor 1%	hairpin (east- west)
	R23	100 Ohm	Resistor 1%	hairpin (north-south)
	R24	100 Ohm	Resistor 1%	Hairpin (south - North)

Install Ceramic Caps

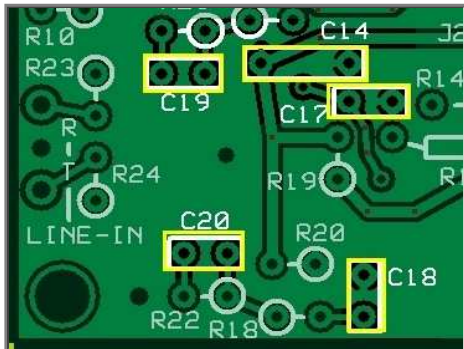
- Install the 5 ceramic capacitors (C14, C17-C20)




Check	Designation	Component Value (code)	Type
	C14	4.7 μ F (code 475)	ceramic
	C17	0.047 μ F (code 473)	ceramic
	C18	0.047 μ F (code 473)	ceramic
	C19	220 pF (code 221)	ceramic
	C20	220 pF (code 221)	ceramic

Completed Stage

[Top](#)

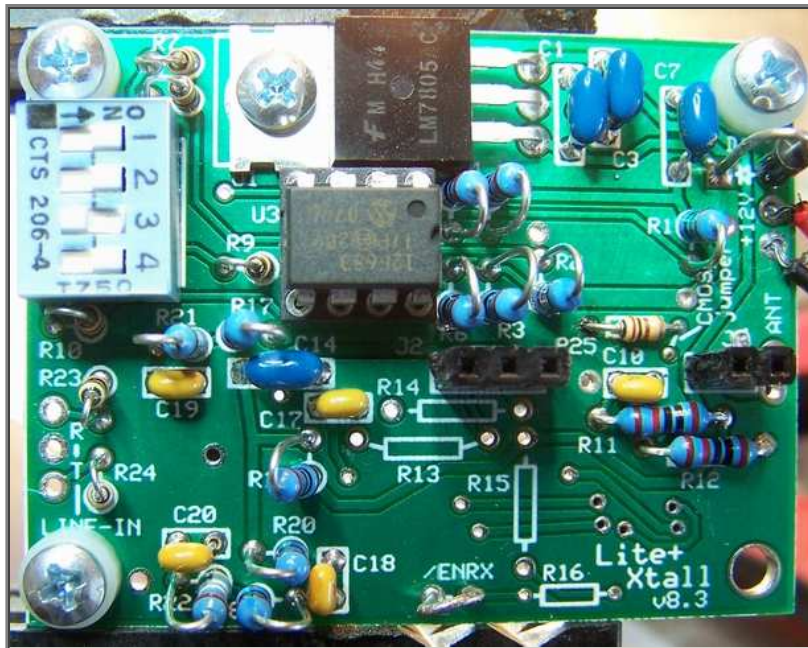

Bottom

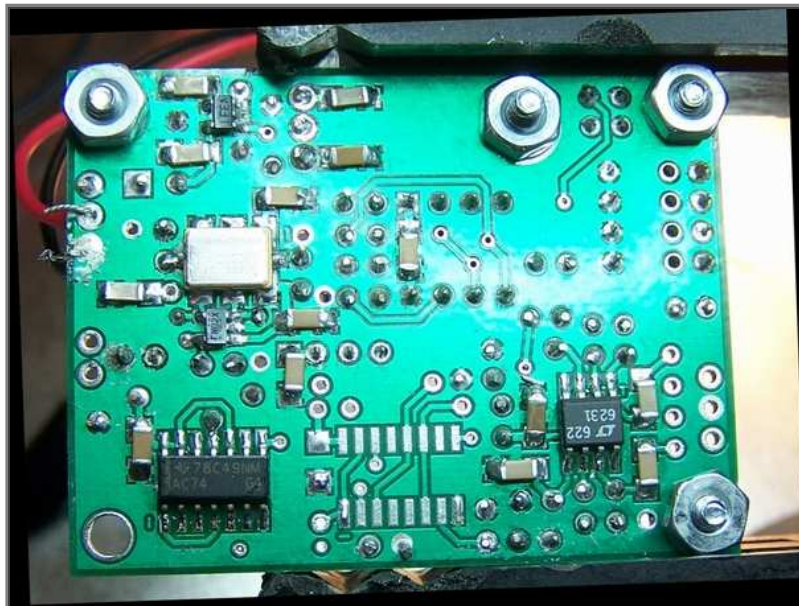

Testing



Current Draw (DMM - 108 mA)

- Remember the 14 mA downward adjustment for the CMOS version of the Si570.
- Set SW1 for a center frequency of 7.046 MHz ("0100")
- Apply power and measure the current with your DVM's ma meter.
- The current draw on the LVDS version of the Si570 should be on the order of 107-108 mA

Current Limited Power Test

- Connect a 100 ohm resistor in series with the power line and apply 12 V dc power
- the current should be relatively low (around 10 mA or less)
- Measure the voltage WRT ground at the +5 V and at the 3.3 Vdc testpoints.
- A voltage of around 2 V dc on each testpoint indicates the power rails are not shorted


Voltage Divider R19/R20 (DMM - 2.5 Vdc)

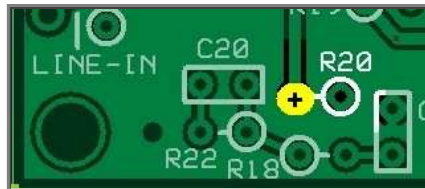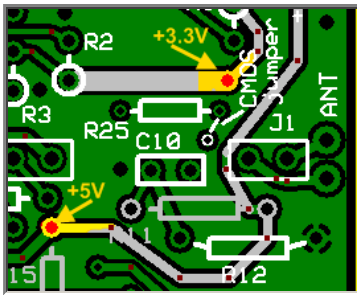

- Measure the voltage at the R20 hairpin lead with respect to ground.
- It should read approximately 2.5 Vdc (½ the 5 volt rail).

Test Point	Units	Expected	Voltage as Measured
R20 hairpin lead	Vdc	2.5	

Pin Voltages (DMM - 5, 2.5, and 0 Vdc)

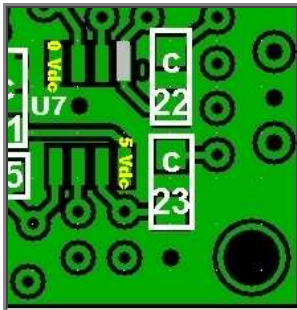

- Measure the voltages at the pins of U7.
- It is best to test for pin voltages at the actual pins (not the pads), thereby ensuring correct soldering of the pins to the pads.


Test Point	Units	Expected	Pin Voltage(s) as Measured
U7, Pins 1, 2, 3, 5, 6 & 7	Vdc	2.5	
U7, Pin 8	Vdc	5	
U7, Pin 4	Vdc	0	

OpAmp Test - DMM (No Scope)

Tony Parks suggested this next test for those who do not have an oscilloscope and/or audio frequency generator, since it requires only a DMM and some clip leads.

The test will test each of the two Op-Amps, but the steps described are for the second Op-Amp and involves R18 and R22. The test for the first Op-Amp involves, respectively, R17 and R21.

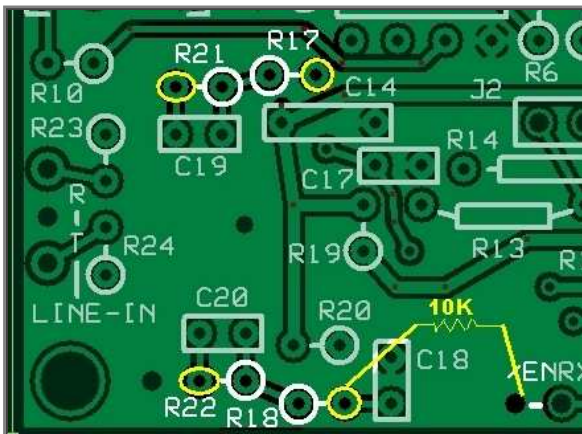If the Op-Amp being tested is working, then the voltage measured at the output of the Op-Amp will increase to accommodate the effect of the changed bias on the input. Passing these tests gives you more than enough confidence to move on to the Mixer stage.




- Obtain a 10k resistor (or use the 10k resistor - R15 - that is to be installed in the next stage)
- using the DMM, measure the dc voltage with respect to ground at the hairpin of R22. The result should be approximately 2.5 Vdc (½ the 5 Vdc rail).
- keep the DMM lead on R22's hairpin
- Using two clip leads, "bridge" the 10k resistor between the hairpin of R18 and ground. See the diagram to the left.
- Observe the voltage reading at R22 hairpin. If OpAmp 1 is working, the voltage should have jumped to approximately 3.75 Vdc
- Remove the resistor/clip lead from R18 and the voltage at R22 should go back to the 2.5 Vdc level.
- Follow these same steps for OpAmp2, substituting R17 for R18 and R21 for R22.

Audio Injection (optional)


(AF Oscillator/Scope/Freq Counter)

- Set up an audio signal generator for a low-level (10 mV p-p) output (you can use the output of IQGen or DQGen or Rocky's TX)
- Connect the audio generator's output, through a 5 µF dc blocking capacitor, to the hairpin lead of either R17 (for the "Q"/"Ring" Output) or R18 (for the "I"/"Tip" output)
- Connect the Scope's CH2 probe to the "Ring" or "Tip" output pad on the board
- Connect the Oscilloscope's CH1 probe to the audio generator's output

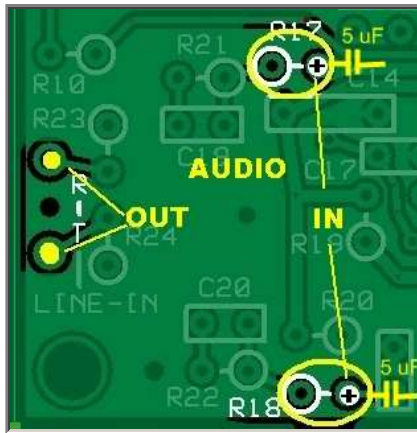

- Op-
- Power up the board and adjust the amplitude of the input signal
 - Measure the output. The gain should be on the order of 5 V p-p (54 dB gain)
 - Repeat the above steps for the other ("Tip" or "Ring") board output

Amp In/Out

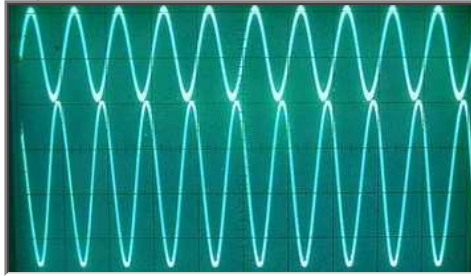

Courtesy of Leonard KC0WOX

[Home Page](#)
[Power Supply](#)
[Local Oscillator](#)
[Dividers](#)
[Op Amps](#)
[BPF\(s\)](#)
[Mixer](#)